

Understanding Frequency Synthesis

By Erik Mentze, Sr. Systems Engineer, Cypress Semiconductor

Configuring a Phase Locked Loop (PLL) for a given frequency synthesis application can be, at the same time, both a quick and easy process as well as a time consuming, tedious, and iterative process. This dual nature in PLL system design arises from the number of loop parameters that need to be appropriately dialed in for a given application. As will be discussed in this article, there are two categories of loop parameters that must be considered: frequency synthesis parameters and performance parameters. The former sets up the loop to generate the correct frequency while the latter dictates the quality of output frequency (with “quality” being a term relative to the given application). The interplay between these two categories of parameters is where designers spend the bulk of their time. After determining a set of frequency synthesis parameters that meet the system needs, we then attempt to dial in the performance parameters. However, when we reach the end of optimizing the loop, there is always the doubt: did I choose the best possible frequency synthesis parameters? Perhaps there is a different set that will run cleaner and consume less power or have more margin. It is these design choices that this paper will attempt to shed some common sense design principles upon.


An Overview of PLL Frequency Synthesis

At the most fundamental level, the goal of any frequency synthesizer is, based on a given reference frequency, to generate a desired output frequency. That is, solve:

$$f_{out} = \kappa \cdot f_{ref} \tag{1}$$

where κ is the frequency scaling constant, sometimes referred to as the normalized frequency. Any frequency synthesizer circuit is simply a mechanism for approximating κ . A PLL frequency synthesizer approximates κ by inserting divide blocks between the reference oscillator and the output clock. Then, using a feedback loop with a phase detector to maintain phase coherence between the two dividers, the desired frequency is generated. The block diagram for this is shown in Figure 1. This is the general form of a charge pump integer divide phase locked loop (a very common topology used for frequency synthesis).

Figure 1. Block diagram of a basic integer divide PLL.

 

Three divide blocks are used to approximate the value of κ : the reference divider (Q), the feedback divider (P), and the output divider (N). It can be readily shown that κ is defined for this type of frequency synthesizer as:

$$\kappa = \frac{P}{Q \cdot N} \tag{2}$$

Combining equations 1 and 2, the relationship between input and output frequency is:

$$f_{out} = \frac{P}{Q \cdot N} \cdot f_{ref} \quad (3)$$

It is these P, Q, and N divide values that we refer to as the “frequency synthesis parameters”. These values setup the gross functionality of the loop and must be chosen to set the desired output frequency. One common way of determining these values is to divide the output frequency by the reference frequency, and reduce the fraction:

$$\frac{f_{out}}{f_{ref}} = \frac{P}{Q \cdot N} \quad (4)$$

The difficulty in solving equation 4, for any arbitrary reference and output frequency, is that there are three degrees of freedom (limited only by the range of divide values P, Q, and N can take on). The most common technique for solving equation 4 is a search algorithms. Such algorithms work by searching the solution space, looking for sets of P, Q, and N values that will result in the desired κ value. They are, in essence, triple nested loops that search all possible P, Q, and N values.

Common simplifications are to set N equal to one, Q equal to one, or both. These simplifications are based on system design needs. Analysis of all three of these simplifications is a subset of the general case shown in figure 1 and represented by equation 4.


If both Q and N are set equal to one, then the maximum resolution of the output frequency is limited to the reference frequency, making it possible to synthesize only integer multiples of the reference. In this case determining the value of P is reduced to a simple matter of arithmetic.

If just Q or N is set equal to one, then only a single configuration exists (with respect to a minimum Q/P or N/P ratio) for synthesizing the desired output. Determining this ratio is then a matter of fraction reduction.

The use of all three divide blocks introduces an added layer of generality to the hardware that enables the direct reuse of the PLL through programming for many different frequency synthesis applications. However, this generality also results in a significantly more complex problem in determining the values of P, Q, and N to use. Specifically, it results in multiple frequency synthesis parameter sets that are valid for a given reference and output frequency, all of which can have drastically different performance characteristics (band width, phase margin, jitter, phase noise, power consumption, etc).

An additional configuration that is commonly used in programmable SoCs is to have multiple output dividers. This allows for the synthesis of multiple outputs at different frequencies. Figure 2 illustrates this configuration. It is important to note that each output is an integer multiple of the VCO frequency. This topology emphasizes the importance of selecting the right VCO frequency so as to maximize the number of system clocks that can be generated off of the single PLL.

Figure 2. Block diagram of a basic integer divide PLL with multiple output dividers.

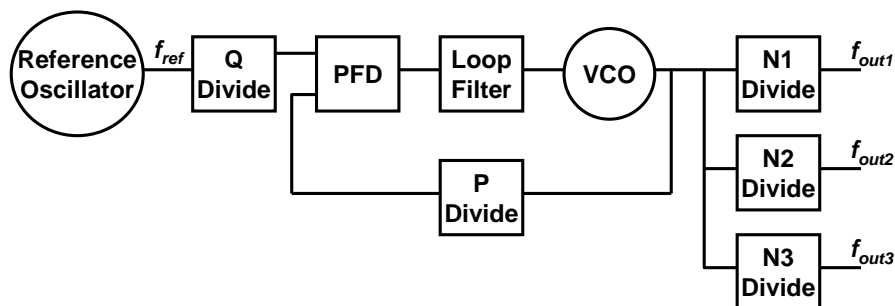

A Quick Walk Around the Loop

With the basic input-output relationship in hand, we next need to take a walk around the PLL and consider the steady-state operating condition. When the loop is in lock, the output of the Q divider and the P divider have matched phase and frequency and the output of the PFD is tri-stated, leaving the loop filter voltage unchanged and the VCO frequency steady. As the loop filter voltage changes (due to noise, charge pump leakage, and capacitor charge leakage), the VCO frequency will drift. The PFD observes this drift by comparing the VCO output to the reference oscillator frequency (through the P and Q dividers respectively) and causes the charge pump to either pump up or pump down the loop filter voltage. Once the correct loop filter voltage is reached again, the PFD output is tri-stated and the loop filter voltage is left unmodified.

During this normal mode of operation, the PFD frequency (the frequency at which the Phase-Frequency Detector runs) plays a central role. The PFD frequency is set by the reference oscillator frequency divided by the reference divider:

$$f_{pfd} = \frac{f_{ref}}{Q} \quad (5)$$

In the steady-state condition, the PLL loop dynamics force the VCO output frequency, divided by the P divider, to also be equal to the PFD frequency:

$$f_{pfd} = \frac{f_{vco}}{P} \quad (6)$$

By re-arranging equations 5 and 6, we can now make a key observation: *the reference frequency and the VCO frequency must both have the PFD frequency as a common divisor:*

$$Q = \frac{f_{ref}}{f_{pfd}}, \quad P = \frac{f_{vco}}{f_{pfd}} \quad (7)$$

Any valid choice of P and Q will result in a PFD frequency that is a common divisor of both the reference frequency and VCO frequency. This allows us to take a fundamentally different approach to determining the P and Q divide values than the fraction reduction method illustrated in equation (4). It is also worth noting that the PFD frequency will also play a central role in the PLL performance parameters, which we will discuss in more detail later. For now, let's look at selecting the P and Q divide values based on the PFD frequency.

Determining P and Q Divide Values Based on the PFD Frequency

Since we know that the PFD frequency must be a common divisor of the reference frequency and VCO frequency, let's choose it to be the *greatest* common divisor. By doing this we will minimize P and Q, and maximize the PFD frequency:

$$Q = \frac{f_{ref}}{GCD(f_{vco}, f_{ref})} \quad (8)$$

$$P = \frac{f_{vco}}{GCD(f_{vco}, f_{ref})} \quad (9)$$

The range of valid VCO frequencies and N divide values is dictated by the following relationship:

$$\frac{f_{vco(\min)}}{f_{out}} \leq N \leq \frac{f_{vco(\max)}}{f_{out}} \quad (10a)$$

and all valid VCO frequencies are found by multiplying the list of N divide values by f_{out} :

$$f_{vco} = f_{out} \cdot N \quad (10b)$$

Thus, given a reference frequency and desired output frequency, we can use equations 8, 9, and 10 to determine all possible sets of frequency synthesis parameters (sets of P, Q and N). There is only one small problem with equations 8 and 9: the Greatest Common Divisor function is only defined on the set of integers. We usually want to synthesis real frequencies, not integer frequencies. This means that we need to make a few mathematical adjustments to equations 8 and 9 to make them useful in practical applications.

This is done by first recognizing that the reference frequency and output frequency are both real numbers, which implies that they can always be represented as ratios of integers:

$$f_{ref} = \frac{\alpha_{ref}}{\beta_{ref}}, f_{vco} = \frac{\alpha_{vco}}{\beta_{vco}} \quad (11)$$

By multiplying both fractions by their denominators we will transform them into integers (since the product of two integers is always an integer):

$$\frac{\alpha_{ref}}{\beta_{ref}} \cdot \beta_{ref} \cdot \beta_{vco} = \alpha_{ref} \cdot \beta_{vco} \quad (12)$$

$$\frac{\alpha_{vco}}{\beta_{vco}} \cdot \beta_{ref} \cdot \beta_{vco} = \alpha_{vco} \cdot \beta_{ref} \quad (13)$$

We then can take the greatest common divisor of the result:

$$GCD(\alpha_{ref} \cdot \beta_{vco}, \alpha_{vco} \cdot \beta_{ref}) \quad (14)$$

This is almost the result we want. It is the GCD of two frequencies that are related to our original reference and VCO frequency. We can get back to the original values by dividing out the term we used to transform them:

$$\frac{GCD(\alpha_{ref} \cdot \beta_{vco}, \alpha_{vco} \cdot \beta_{ref})}{\beta_{ref} \cdot \beta_{vco}} \quad (15)$$

This result is equal of the greatest common divisor of our original reference frequency and VCO frequency. If we define a function called the greatest common divisor of rational numbers (GCDR) as:

$$GCDR(f_{ref}, f_{vco}) = \frac{GCD(\theta \cdot f_{ref}, \theta \cdot f_{vco})}{\theta} \quad (16)$$

where

$$\theta = LCM(den(f_{ref}), den(f_{vco})) \quad (17)$$

(note that LCM is the Least Common Multiple and *den* is the denominator part of f_{ref} and f_{vco} respectively), then we can solve for P and Q using the following equations:

$$Q = \frac{f_{ref}}{GCDR(f_{vco}, f_{ref})} \quad (18)$$

$$P = \frac{f_{vco}}{GCDR(f_{vco}, f_{ref})} \quad (19)$$

By solving these equations for all VCO frequencies found in equation 10, the set of all divide values that will synthesize our desired output frequency from our given reference frequency is found.

This, however, is a lot of symbols; let's now look at an illustrative example.

An Illustrative Example

For this example, we will synthesize a 50MHz output from a 14.3181818...MHz reference (a common video frequency). Assume the VCO has a frequency range of 100MHz to 400MHz.

First, all possible N divide values are determined using (10):

$$2 = \frac{100MHz}{50MHz} \leq N \leq \frac{400MHz}{50MHz} = 8$$

Based on this list of N divide values, the corresponding VCO frequencies can be solved for and then the Q and P values can be solved for using (18) and (19). For N = 2, the following calculations are made:

1. $N = 2$

2. $f_{ref} = 14.3181818... = \frac{315}{22}$

3. $f_{vco} = 50 \cdot 2 = \frac{100}{1}$

4. $\theta = LCM\left(\text{den}\left(\frac{315}{22}\right), \text{den}\left(\frac{100}{1}\right)\right) = LCM(22, 1) = 22$

5. $Q = \frac{f_{ref}}{f_{PFD}} = \frac{f_{ref}}{GCDR(f_{vco}, f_{ref})} = \frac{\frac{315}{22}}{\frac{GCD\left(\left(\frac{315}{22} \cdot \theta\right), (100 \cdot \theta)\right)}{\theta}} = \frac{315}{5} = 63$

6. $P = \frac{f_{vco}}{f_{PFD}} = \frac{f_{vco}}{GCD(f_{vco}, f_{ref})} = \frac{\frac{100}{1}}{\frac{GCD\left(\left(\frac{315}{22} \cdot \theta\right), (100 \cdot \theta)\right)}{\theta}} = \frac{100}{5/22} = 440$

All results for this example (N=2 through N=8) are shown in table 1. This is the complete set of frequency synthesis parameters that are possible given our reference frequency and desired output frequency.

Table 1. Summary of Example Results

N	Fref [MHz]	fvco [MHz]	Fout [MHz]	f _{pdf} [MHz]	Q	P
2	14.318...	100	50	0.227	63	440
3	14.318...	150	50	0.682	21	220
4	14.318...	200	50	0.227	63	880
5	14.318...	250	50	0.227	63	1100
6	14.318...	300	50	0.682	21	440
7	14.318...	350	50	1.591	9	220
8	14.318...	400	50	0.227	63	1760

Choosing an Optimal Configuration

Now that we have confidently found the set of all possible frequency synthesis parameters that meet our needs, we can turn our attention to selecting the performance parameters. Several common parameters that are optimized in various applications are: power consumption, startup time, settling time, jitter, and phase noise. Table 2 summarizes these parameters, the corresponding key loop parameters, the design equations needed for tradeoffs, and the how to optimize them. It is important to note the role that PFD frequency plays in each of these parameters.

Power

Power is dominated by the VCO frequency, charge pump current, and divide block settings. Most VCO architectures require larger tail currents to achieve higher frequencies. So as frequency increases, so does power consumption. Charge pump current is discharged once for each PFD period. When larger charge pump currents are required (for loop stability or fast startup / settling time) more power is consumed per PFD period. Clock dividers dissipate power at each clock edge. Larger clock divide values require more divide cells to transition, consuming more power.

Startup Time / Settling Time

The startup and settling time for a charge pump PLL is dominated by the loop natural frequency. This parameter can be thought of as the frequency slew rate of the PLL. It quantifies how fast the PLL can change the output frequency. It is proportional to the VCO gain and charge pump current, and inversely proportional to the feedback divide value and loop filter capacitance. Since the PLL output frequency is set by the VCO frequency, when we want to force a large step in the output frequency (either from zero at startup or from one setting to another) we need to force a large step in the VCO control voltage. This is accomplished by the charge pump dumping a large amount of charge onto the loop filter cap. The amount of frequency change per volt increase on the loop filter is set by the VCO gain. The rate at which the loop filter voltage is updated is set by the PFD frequency.

Jitter (Cycle-to-Cycle)

Cycle-to-Cycle jitter (the change in period length from one period to the next) can easily be dominated by the individual blocks of the PLL (VCO, dividers, reference oscillator), creating a situation where no loop parameter changes can improve performance. If you are working with a low noise PLL, then loop parameter settings can make a significant improvement.

Similar to startup time / settling time, the PFD frequency and VCO gain play a key role. Higher PFD frequencies mean that the PLL loop filter voltage is refreshed at a higher rate. This prevents the loop filter voltage from drifting. By using a large loop filter capacitance, the amount of voltage drift per PFD period is minimized. Because the VCO gain dictates how far the output frequency drifts per unit voltage drift on the loop filter, lower VCO gain makes the PLL less sensitive to loop filter voltage drift.

Phase Noise

Optimizing phase noise is highly application dependent, but a few general observations can be made. Phase noise contributed by the reference oscillator can be suppressed by setting the PLL to a lower closed loop bandwidth. Phase noise contributed by the VCO can be suppressed by setting the PLL to a higher closed loop bandwidth.

Phase noise divides down proportional to the output divide setting. If the output divider is a low noise divider, then running the VCO at a higher frequency and dividing the output frequency down will result in a phase noise improvement.

Table 2. Summary of key PLL performance parameters

Parameter	Key Loop Parameters	Key Design Equations	Optimization
Power	VCO frequency (f_{vco}) PFD Frequency (f_{pfd}) Charge pump Current (I_{chp}) Divide Values (P, Q, N)	$f_{vco} = f_{out} \cdot N$ $\omega_n = \sqrt{\frac{K_{VCO} I_{CP}}{P \cdot (C_L + C_S)}}$	Minimize f_{vco} Minimize I_{chp} Minimize f_{pfd} Minimize P, Q, N
Startup Time Settling Time	PFD Frequency (f_{pfd}) Charge Pump Current (I_{chp}) Loop Filter Capacitance (C) VCO Gain (K_{vco})	$f_{pfd} = \frac{f_{ref}}{Q}$ $\omega_n = \sqrt{\frac{K_{VCO} I_{CP}}{P \cdot (C_L + C_S)}}$	Maximize f_{pfd} Maximize I_{chp} Minimize C Maximize K_{vco}
Jitter (cycle-to-cycle)	PFD Frequency (f_{pfd}) Loop Filter Capacitance (C) VCO Gain (K_{vco})	$f_{pfd} = \frac{f_{ref}}{Q}$ $\omega_n = \sqrt{\frac{K_{VCO} I_{CP}}{P \cdot (C_L + C_S)}}$	Maximize f_{pfd} Maximize C Minimize K_{vco}
Phase Noise	Closed Loop Bandwidth PLL Component Phase Noise	$H(s) = \frac{G(s)}{1 + G(s)}$ $E(s) = \frac{1}{1 + G(s)}$	Depends on component noise figures. Use loop bandwidth to suppress reference noise and VCO noise.

ω_n = natural frequency
 K_{vco} – VCO gain (Hz/V)
 I_{chp} – charge pump current (A/rad)
 C_L, C_S – Loop filter large cap, and loop filter small cap respectively
 $H(s)$ – closed loop transfer function
 $G(s)$ – open loop transfer function
 $E(s)$ – error transfer function

Optimizing the Illustrative Example

Finally let’s apply this general discussion on optimization to the list of PLL configurations that we found in the above example.

Power

If low power consumption is the primary design concern we want to minimize VCO frequency and divide values. Selecting N=3, Q=21, P=220 would be the best choice. This operates the VCO at one of the lower frequencies, lower P and Q values, and has a reasonable PFD frequency.

Startup / Settling Time

If startup / settling time is the primary concern, then from table 1 it is clear that the N=7, Q=9, P=220 is the most desirable. It has an f_{PFD} of more than two times any other configuration, resulting in a higher refresh rate on the loop filter voltage.

Jitter

If low jitter is the primary concern, then N=7, Q=9, P=220 is again the most desirable. It has an f_{PFD} of more than two times any other configuration, resulting in a higher refresh rate on the loop filter voltage and the lowest jitter of all the



possible configurations.

Phase Noise

Optimizing phase noise is highly application dependent and depends on specific reference oscillator and VCO noise performance. The one design choice we can make based on our configuration list is to choose a high VCO frequency that is divided down. $N=7$, $Q=9$, $P=220$ is probably the best because its PFD frequency is so much higher than $N=8$, $Q=63$, $P=1760$. If the loop has high jitter, then the phase noise floor will rise significantly, swamping out any improvement the output divider is giving us.

Conclusion

Configuring a PLL for system applications can be an arduous task with lots of iteration. By first solving for all frequency synthesis parameters that meet our needs, we can then make well founded design choices that maximize flexibility and minimize cost.

Cypress Semiconductor
198 Champion Court
San Jose, CA 95134-1709
Phone: 408-943-2600
Fax: 408-943-4730
<http://www.cypress.com>

© Cypress Semiconductor Corporation, 2007. The information contained herein is subject to change without notice. Cypress Semiconductor Corporation assumes no responsibility for the use of any circuitry other than circuitry embodied in a Cypress product. Nor does it convey or imply any license under patent or other rights. Cypress products are not warranted nor intended to be used for medical, life support, life saving, critical control or safety applications, unless pursuant to an express written agreement with Cypress. Furthermore, Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress products in life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

PSoC Designer™, Programmable System-on-Chip™, and PSoC Express™ are trademarks and PSoC® is a registered trademark of Cypress Semiconductor Corp. All other trademarks or registered trademarks referenced herein are property of the respective corporations.

This Source Code (software and/or firmware) is owned by Cypress Semiconductor Corporation (Cypress) and is protected by and subject to worldwide patent protection (United States and foreign), United States copyright laws and international treaty provisions. Cypress hereby grants to licensee a personal, non-exclusive, non-transferable license to copy, use, modify, create derivative works of, and compile the Cypress Source Code and derivative works for the sole purpose of creating custom software and or firmware in support of licensee product to be used only in conjunction with a Cypress integrated circuit as specified in the applicable agreement. Any reproduction, modification, translation, compilation, or representation of this Source Code except as specified above is prohibited without the express written permission of Cypress.

Disclaimer: CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS MATERIAL, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. Cypress reserves the right to make changes without further notice to the materials described herein. Cypress does not assume any liability arising out of the application or use of any product or circuit described herein. Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress' product in a life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

Use may be limited by and subject to the applicable Cypress software license agreement.