



**Please note that Cypress is an Infineon Technologies Company.**

The document following this cover page is marked as “Cypress” document as this is the company that originally developed the product. Please note that Infineon will continue to offer the product to new and existing customers as part of the Infineon product portfolio.

**Continuity of document content**

The fact that Infineon offers the following product as part of the Infineon product portfolio does not lead to any changes to this document. Future revisions will occur when appropriate, and any changes will be set out on the document history page.

**Continuity of ordering part numbers**

Infineon continues to support existing part numbers. Please continue to use the ordering part numbers listed in the datasheet for ordering.



## Terminating RoboClock II™ Output

### **Abstract**

This document describes the methods available for terminating the output for the RoboClock II family of products. It also weighs the benefits of each method.

### **Introduction**

The RoboClock II™ family of products consists of high-speed multi-phase PLL clock buffers that offer user-selectable control over system clock functions. This multiple output clock driver gives the system integrator the functions necessary to optimize the timing of high-performance computer and communication systems. The RoboClock II family includes the following parts: CY7B993V, CY7B9930V, CY7B994V, CY7B9940V, and CY7B9945V.

### **Why RoboClock II Output must be Terminated**

Transmission line effects are present on all electrical interconnections. However, these effects become a real concern only with increasing rising and falling edge rates. Given the typical operating frequencies of RoboClock II systems, a clear understanding of transmission effects is paramount to proper implementation of the part. This document describes transmission line effects and how to accommodate them in your design.


### **When Does a Trace become a Transmission Line?**

The first step in any analysis is to determine whether your interconnection can be treated as a simple trace or whether you have to adopt transmission line rules. A good rule of thumb involves comparing the rise time of the driver to the propagation delay of the trace you are driving. If the round trip delay of the trace (twice the propagation delay) is greater than the faster of the rise or fall time, the transmission line effects will not be masked by the rising (falling) edge of the driving device. Thus, the rise (fall) time and propagation delay of the trace are important elements in transmission line analysis.

### **Transmission Line Effects on Clock Signals**

The transmission line effects are caused by impedance mismatch. These impedance mismatches occur because of impedance differences between the driver, trace, and load. They can also be caused by discontinuities (such as vias, stubs, and different loading) along the transmission line. Any time the impedance along a transmission line changes, a reflection will occur. Reflections cause ringing, which is voltage overshoot and undershoot above and below the final state of the signal (see Figure 1). One way to work around the effects of ringing is to wait until the voltage levels have stabilized. This, however, requires the addition of extra clock cycles and can slow down a system considerably. The unwelcome overshoot due to reflections can cause latch-up in a sensitive system. The unwanted over and undershoot will radiate larger fields, thus transferring more crosstalk to neighboring traces. The ringing can also reduce noise margin and induce false clocking.


Figure 1. Transmission Line Effects

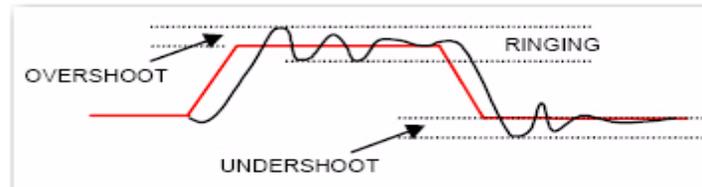

### Sample Transmission Line Calculation

As stated, the two critical parameters that must be analyzed when determining whether to treat a trace as a transmission line are the rising (and falling) time of the driver and the propagation delay of the trace being driven. The rise and fall times of the driver will usually be listed in the device datasheet. The propagation delay for the trace can be calculated using the appropriate formula for the respective transmission line type. The following is a typical analysis for a PCB board with microstrip traces.

Figure 2. Microstrip

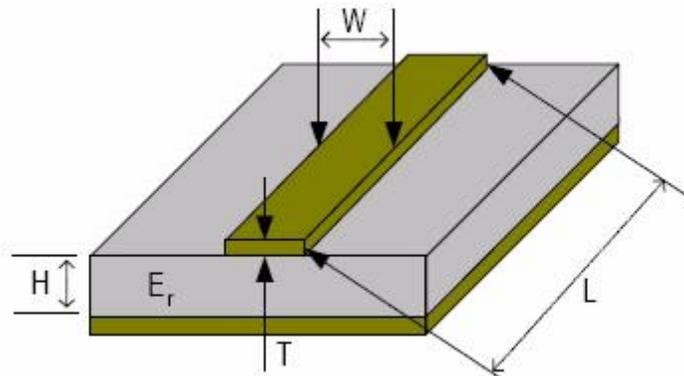

Assume a 5-in microstrip line is being driven by a RoboClock II output with a rise time of 1 ns. The line is loaded at the end with one device. The load adds 20 pF of capacitance. Is termination required in this instance?

Given  $W = 0.008$  in,  $H = 0.005$  in,  $T = 0.0025$  in,  $L = 5.000$  in, and  $ER = 4.6$ , calculate the impedance and propagation delay of the microstrip trace:

$$Z_0 = \frac{87}{\sqrt{ER+1.41}} \ln\left(\frac{5.98H}{0.8W+T}\right) = 43.03\text{ohms}$$

$$t_{PD} = 1.017\sqrt{0.475ER+0.67} = 1.718\text{ns/ft} = 0.143\text{ns/in}$$

This is the new one-way propagation delay for the 5-in trace. The round trip delay is  $2 \times t_{PD}$ , 3.436 ns/ft. Again, the trace must be treated as a transmission line if:

$$2 \times t_{PD} \times \text{TRACELENGTH} \geq t_{RISE}$$

$$2 \times t_{PD} \times \text{TRACE LENGTH} = 2 \times 1.718\text{ns/ft} \times 5/12\text{ft} = 1.432\text{ns}$$

Because 1.432 ns is greater than the rise time of the output buffer (1 ns), the trace must be treated as a transmission line and termination is required.


### Termination Techniques

Transmission line theory states that a signal sent down a transmission line that has constant characteristic impedance will propagate undistorted along the line. At the load a voltage reflection will occur if the load impedance is not equal to that of the line. The goal of transmission line termination is to match the source and/or load impedance to that of the transmission line. This ensures an optimal delivery of the signal to the load. There are several methods of transmission line termination, all with their own advantages and disadvantages. The two most popular termination techniques used with clock lines are Thevenin termination and series termination.

#### Thevenin Termination

Thevenin termination attempts to match the load impedance with that of the transmission line. It uses a pull-up and pull-down resistor to achieve this (see Figure 3). The Thevenin equivalent resistance is set equal to the characteristic impedance of the trace,  $Z_0$ . A disadvantage of this termination technique is the DC current path from  $V_{CC}$  to GND through the termination. Thevenin termination also uses more components than series termination.


Figure 3. Thevenin Termination

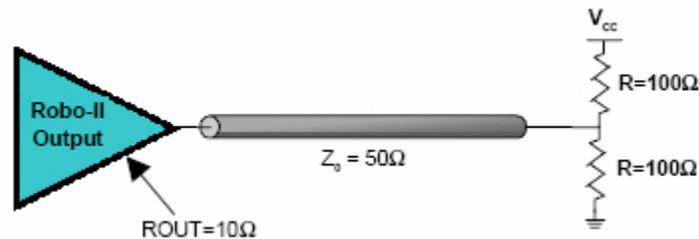

#### Series Termination


The objective of series termination is to match the source impedance with that of the transmission line. The value of the series resistor is chosen such that the series combination of the output impedance of the source driver and the series resistor is equal to the characteristic impedance of the transmission line. This configuration will then absorb any reflections from the load. However, this works only if there is a no DC load. This may not be as straightforward as it seems, because drivers can have different HIGH-to-LOW and LOW-to-HIGH output impedance. The RoboClock II output buffer is designed to have the same output impedance when driving both HIGH and LOW. This is typically about 10  $\Omega$ . Series termination is a good choice when power dissipation is critical and the load is a capacitive load. With this termination, however, loads must be located at the end of the trace. The series terminating resistor should be placed as close as possible to the RoboClock II output.

Figure 4. Series Termination

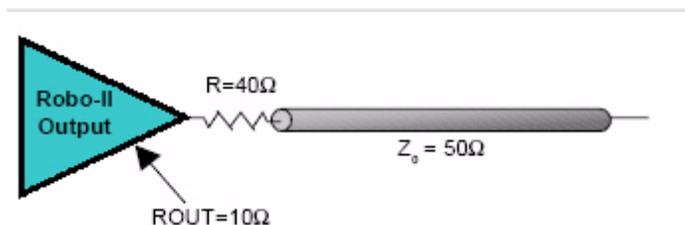

Either Thevenin termination and series termination can be used to terminate RoboClock II output. The datasheet specifications are quoted and tested based on the Thevenin termination. Thus, specifications may vary slightly for different termination techniques.

Figure 5. Multi-Series Termination

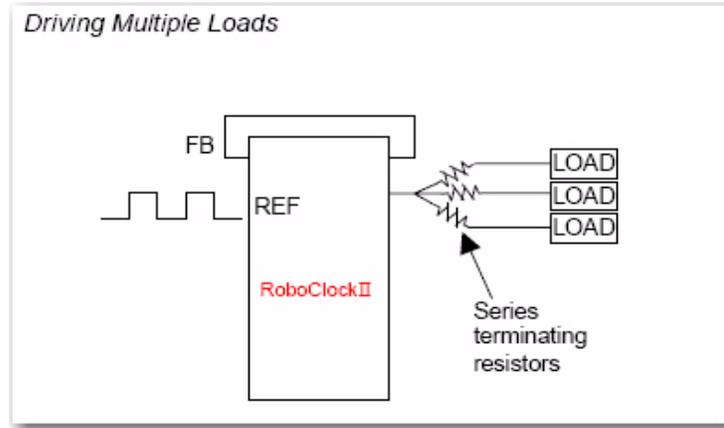


For point-to-point connections, either series or Thevenin termination suffices. However, when driving multiple loads, series termination should be used. A star network should be configured with a series-terminating resistor for each load as illustrated in Figure 5. The value of the series resistor in this case is calculated using the following equation:

$$R_{\text{SERIES}} = Z_0 - \left( \frac{10}{\text{Number of Traces}} \right)$$

If layout constraints prohibit this, or if you are daisy chaining loads, the configuration in Figure 6 should be used. Note the resistor values in this instance should be about 100  $\Omega$ . Thevenin termination should not be used if you are driving three or more loads. This is because the effective resistance of the combined termination may be too low for the driver to drive.

Figure 6. Alternative Method for Terminating Multiple Loads

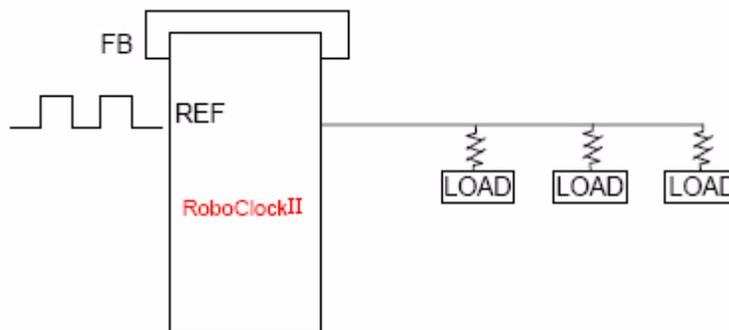


### Effects of Capacitive Load

When a trace is loaded with devices, the load capacitance adds to the trace's capacitance. A heavily loaded trace slows the rise and fall times of the driver due to the increased RC time constant associated with the load capacitance.

The RoboClockII output is designed to drive a capacitive load of up to 25 pF. The effects of capacitive load on the rise time of the output buffers are illustrated in Figure 7, which compares a RoboClock II output buffer driving a 0-pF load and a 25-pF load.


Figure 7. Loaded Versus Unloaded Output

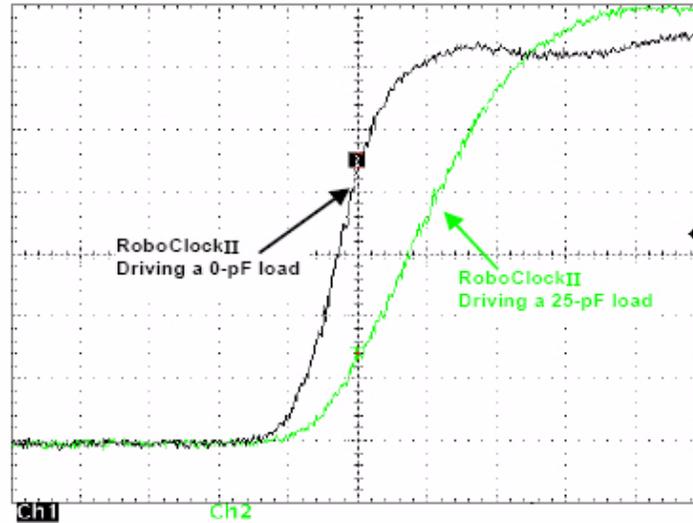

This 'scope waveform compares the rise time of an output loaded with a 25-pF load to that of an unloaded output. The loaded output has a rise time of 650 ps whereas the unloaded output has a rise time of 310 ps.

The datasheet is specified for an output load of 25 pF or less. The effects of capacitive load on rise time are graphed in Figure 8. You can use this graph to determine the effects of your capacitive load on the output buffer's rise time under quiescent operating conditions.

Figure 8. Capacitive Load versus Rise Time

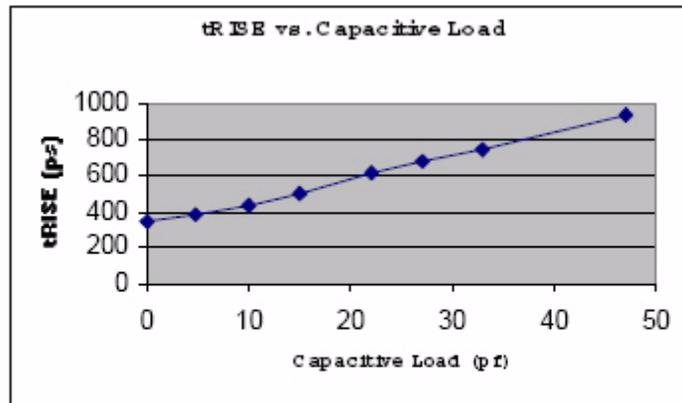

This graph shows the effects of capacitive load on rise time. The data here is for typical silicon operating at 24 MHz, at room temperature with a 3.3V  $V_{CC}$ .

## Summary

Proper clock output termination is important to provide the best possible signal integrity at the receiver. There are a few types of termination options available to the system designer. The different termination types and their advantages and disadvantages have been discussed here. The system designer should take these factors into account when deciding how to best terminate clock signals.

Cypress Semiconductor  
198 Champion Court  
San Jose, CA 95134-1709  
[www.cypress.com](http://www.cypress.com)

© Cypress Semiconductor Corporation, 2010-2017. This document is the property of Cypress Semiconductor Corporation and its subsidiaries, including Spansion LLC ("Cypress"). This document, including any software or firmware included or referenced in this document ("Software"), is owned by Cypress under the intellectual property laws and treaties of the United States and other countries worldwide. Cypress reserves all rights under such laws and treaties and does not, except as specifically stated in this paragraph, grant any license under its patents, copyrights, trademarks, or other intellectual property rights. If the Software is not accompanied by a license agreement and you do not otherwise have a written agreement with Cypress governing the use of the Software, then Cypress hereby grants you a personal, non-exclusive, nontransferable license (without the right to sublicense) (1) under its copyright rights in the Software (a) for Software provided in source code form, to modify and reproduce the Software solely for use with Cypress hardware products, only internally within your organization, and (b) to distribute the Software in binary code form externally to end users (either directly or indirectly through resellers and distributors), solely for use on Cypress hardware product units, and (2) under those claims of Cypress's patents that are infringed by the Software (as provided by Cypress, unmodified) to make, use, distribute, and import the Software solely for use with Cypress hardware products. Any other use, reproduction, modification, translation, or compilation of the Software is prohibited.

TO THE EXTENT PERMITTED BY APPLICABLE LAW, CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS DOCUMENT OR ANY SOFTWARE OR ACCOMPANYING HARDWARE, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. To the extent permitted by applicable law, Cypress reserves the right to make changes to this document without further notice. Cypress does not assume any liability arising out of the application or use of any product or circuit described in this document. Any information provided in this document, including any sample design information or programming code, is provided only for reference purposes. It is the responsibility of the user of this document to properly design, program, and test the functionality and safety of any application made of this information and any resulting product. Cypress products are not designed, intended, or authorized for use as critical components in systems designed or intended for the operation of weapons, weapons systems, nuclear installations, life-support devices or systems, other medical devices or systems (including resuscitation equipment and surgical implants), pollution control or hazardous substances management, or other uses where the failure of the device or system could cause personal injury, death, or property damage ("Unintended Uses"). A critical component is any component of a device or system whose failure to perform can be reasonably expected to cause the failure of the device or system, or to affect its safety or effectiveness. Cypress is not liable, in whole or in part, and you shall and hereby do release Cypress from any claim, damage, or other liability arising from or related to all Unintended Uses of Cypress products. You shall indemnify and hold Cypress harmless from and against all claims, costs, damages, and other liabilities, including claims for personal injury or death, arising from or related to any Unintended Uses of Cypress products.

Cypress, the Cypress logo, Spansion, the Spansion logo, and combinations thereof, WICED, PSoC, CapSense, EZ-USB, F-RAM, and Traveo are trademarks or registered trademarks of Cypress in the United States and other countries. For a more complete list of Cypress trademarks, visit [cypress.com](http://cypress.com). Other names and brands may be claimed as property of their respective owners.