



Please note that Cypress is an Infineon Technologies Company.

The document following this cover page is marked as “Cypress” document as this is the company that originally developed the product. Please note that Infineon will continue to offer the product to new and existing customers as part of the Infineon product portfolio.

Continuity of document content

The fact that Infineon offers the following product as part of the Infineon product portfolio does not lead to any changes to this document. Future revisions will occur when appropriate, and any changes will be set out on the document history page.

Continuity of ordering part numbers

Infineon continues to support existing part numbers. Please continue to use the ordering part numbers listed in the datasheet for ordering.

Generating a Power-Fail Interrupt using the F-RAM Processor Companion

Author: Harsha Medu

Associated Part Family: FM31256, FM3164, FM31278, FM31276
 FM31L278, FM31L276, FM33256B

Related Application Notes: [click here](#)

AN400 describes the implementation of an early power-fail warning using the general-purpose comparator on the F-RAM Integrated Processor Companion. This warning signal can be used to drive a microcontroller interrupt input.

1 Overview

The F-RAM integrated Processor Companion features a general-purpose comparator that can be used to generate an early power-fail interrupt (PFI). This warning signal can drive a microcontroller interrupt input and must occur before V_{DD} drops too low to save all critical data to the nonvolatile RAM. The Processor Companion's early power-fail interrupt can also be used as a warning to the system to stop conducting critical activity during a brownout condition.


1.1 Power Supply Monitoring

The power supply can be monitored using the F-RAM Processor Companion family of products. The FM31xxx family is an I²C interface product and the FM33xxx family is an SPI interface product. As shown in Figure 1, an analog comparator compares the PFI input pin to an onboard reference voltage. When the PFI input voltage drops below the reference threshold, the comparator will drive the PFO output pin (ACS pin on FM33xxx and CAL/PFO pin on FM31xxx) to a LOW state. This early power-fail warning can be used as a system interrupt for a host microcontroller. This application note shows two implementations using this comparator. The FM31xxx family is used in this document.

Note: The FM33xxx comparator is similar to FM31xxx, except for a change in the comparator reference voltage. The reference voltage in the FM33xxx is 1.5 V, while it is 1.2 V in the FM31xxx comparator.


In a typical system, the comparator's output is tied to the non-maskable interrupt (NMI) input of a microcontroller as shown in Figure 1. The comparator provides a single input (PFI pin) for monitoring voltage. The other comparator input is tied to an on-board 1.2-V precision reference (1.5 V in FM33xxx). Since the comparator is non-inverting, the output will drive to a low state when the PFI input drops below 1.2 V. To use this function as a PFI, the PFI input should be connected to the power supply voltage to be monitored through a voltage divider.

Figure 1. System Hookup and Monitor Point

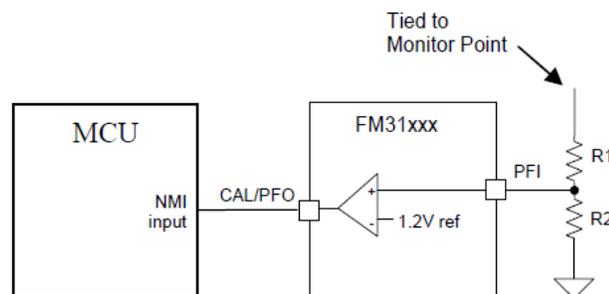


First Method: AC line-operated systems use voltage-regulated power to provide a stable voltage to guarantee circuit operation. The regulator is always preceded by an unregulated power supply. As the unregulated voltage varies, the regulated voltage remains stable – to a point. Hence, during a power failure or system shutdown, the unregulated supply voltage will begin to drop before the regulated output (V_{DD}) is affected. Therefore, by generating a NMI when the unregulated power supply voltage drops below a threshold, the processor and the memory subsystem know that power will be lost well before the regulator drops out. A common line-operated power supply that is well suited to this type of application is shown in Figure 2.

Figure 2. Line-Operated Power Supply

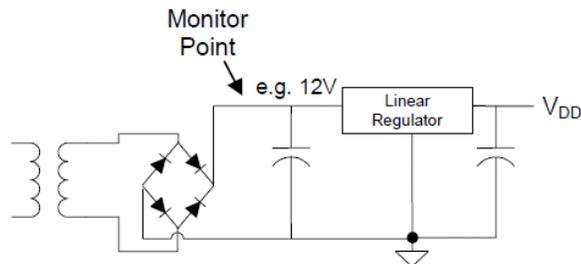

Second Method: A regulated LDO output (V_{DD}) can be monitored for a drop below a selected threshold so that the interrupt occurs at a higher voltage than the processor reset trip point. A typical battery-based power supply that is suited to this approach is shown in Figure 3.

Figure 3. Battery-based Power Supply

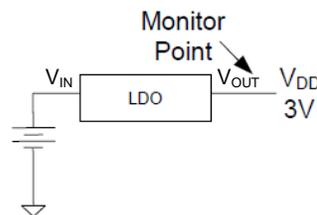

In the first method, the interrupt is generated in response to a voltage drop on the regulator's unregulated side, that is, 12 V in the example application given in Figure 2. This will occur well before the regulated output (V_{DD}) drops. In the second method, the power supply is a primary battery with a low dropout (LDO) regulator. The LDO output may begin to drop soon after the battery voltage falls, so it can more accurately monitor V_{DD} directly. Most LDO regulators exhibit a linear relationship between V_{IN} and V_{OUT} when V_{IN} drops below V_{OUT} .

The early power-fail comparator can support either approach, but the first method provides a warning much earlier.

In the case of monitoring an unregulated power supply (first method), power loss due to a brownout condition and complete power down are shown in Figure 4. An interrupt is generated well before V_{DD} drops because the monitored voltage occurs at an earlier point in the power supply. In the case of a primary battery (second method) shown in

Figure 5, V_{DD} is directly monitored and there is no brownout case.

To trigger the NMI, as shown in Figure 4, the NMI trip point must be carefully chosen. The goal is to generate an NMI signal as soon as possible when power drops, but not generate an NMI within the normal tolerance or ripple of the power supply, yet not so late that the voltage regulator starts to drop out.

Figure 4. Power-down Events for Line-Operated Supply


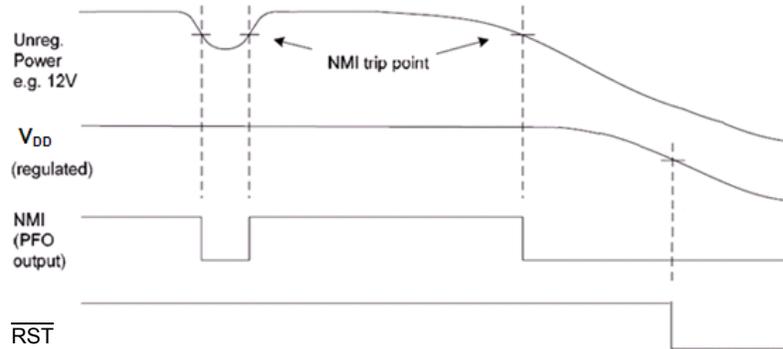


Figure 5. Power-down Events for Battery Supply

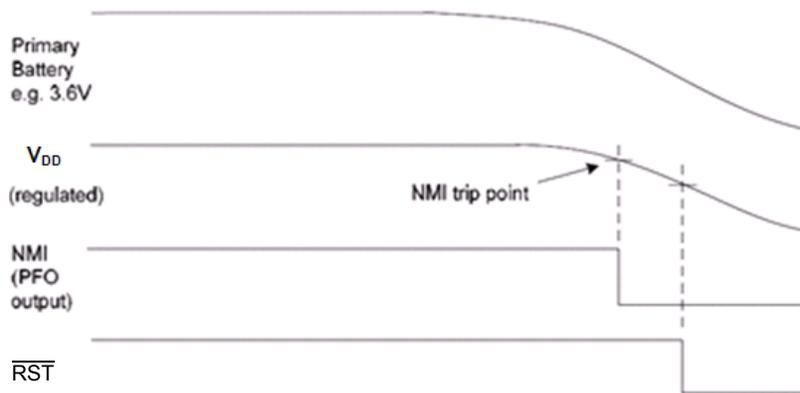

Example: A 12-V power supply with a $\pm 10\%$ tolerance is allowed a 10.8-V output level; therefore, the PFO pin should be set to trip no higher than 10.3 V to provide an additional 0.5-V margin. A lower limit on the supply trip point is the minimum V_{IN} specification for the linear regulator. A LDO regulator requires very little headroom whereas a conventional linear regulator needs more input voltage. For example, a 5-V linear regulator may have a dropout specification of 2 V, meaning that V_{OUT} , or system V_{DD} , will begin to drop when the input voltage reaches 7 V. Therefore, in this example, the PFO trip point should be set between 10.3 V and 7 V.

The power supply sense circuit is a simple voltage divider, tied to the unregulated supply with the tap point connected to the PFI pin, which is the input to the on-chip comparator. The resistor values are chosen to generate an NMI when the divided voltage on the PFI input goes below the 1.2-V comparator reference (1.5 V for FM33xxx). The trip point is defined by a simple resistor divider ratio.

Note: Ensure the PFI pin voltage level cannot exceed V_{DD} (min).

The equation is:

$$V_{TRIP} \times \frac{R2}{R1 + R2} = 1.2 \text{ V}$$

For example, if the power supply is 12 V $\pm 10\%$, the regulated output V_{DD} is 5 V $\pm 10\%$, and the desired NMI trip point V_{TRIP} is 9 V, then the divider ratio $R2 / (R1 + R2)$ is 0.133.

Note: Resistors R1 and R2 are labeled in [Figure 1](#).

$$\text{We know, } 0.133 = \frac{R2}{R1 + R2}$$

$$\text{And, } R1 + R2 = \frac{R2}{0.133}$$

$$\text{So, } R1 = \frac{R2}{0.133} - R2$$

For $R2 = 47 \text{ k}\Omega$, $R1 = 306 \text{ k}\Omega$

The easiest solution is to choose one resistor and then solve for the other.

2 Additional Considerations

The slew rate of the power supply on the unregulated side can dictate the amount of time that is available for backing up data after an NMI occurs and before a reset occurs. For example, assume the nominal 12-V supply has a slew rate of 0.5 V/ms. In this example, an NMI is generated at 9 V, and the 5-V linear regulator begins to drop out at 7 V. The NMI will occur 4 ms before the regulator drops out causing the F-RAM Processor Companion V_{DD} input level to drop. The comparator is a convenient way to generate an interrupt, which provides enough time for the processor to save critical data to the nonvolatile RAM. It can also be used to poll the power conditions. After the NMI occurs, it is advisable to monitor the signal continuously and to avoid conducting critical activity until the NMI clears. If the NMI is the result of a brownout, then eventually the condition will clear and normal operation can resume. If it is not a brownout, the reset pin ($\overline{\text{RST}}$) will eventually be asserted.

3 Summary

From this application note it is clear that system designers can use the F-RAM Processor Companion for dual purposes in a system. In addition to being an F-RAM nonvolatile memory, it can be used to generate a power-fail interrupt to the host controller, which eliminates a separate power-fail detection circuit. A well-implemented early power-fail detection signal can give the host controller enough time to prepare the system for a power down.

4 Related Application Notes

You can refer to the following application notes for better understanding of the F-RAM Processor Companion devices.

- [AN407 - A Design Guide to I2C F-RAM Processor Companions – FM31278, FM31276, FM31L278, and FM31L276](#)
- [AN408 - A Design Guide to SPI F-RAM Processor Companion - FM33256B](#)
- [AN401 – Charging Methods for the F-RAM RTC Backup Capacitor](#)
- [AN402 - F-RAM RTC Oscillator Design Guide](#)
- [AN404 - F-RAM RTC Backup Supply \(\$V_{BAK}\$ pin\) and UL Compliance](#)

Document History

Document Title: AN400 – Generating a Power-Fail Interrupt using the F-RAM Processor Companion

Document Number: 001-87076

Revision	ECN	Orig. of Change	Submission Date	Description of Change
**	4018188	MEDU	06/07/2013	New Spec.
*A	4541202	MEDU	11/06/2014	Changed title from "Generating a Power-Fail Interrupt using the F-RAM Processor Companion Power-Fail Comparator" to "Generating a Power-Fail Interrupt using the F-RAM Processor Companion". Added Related Application Notes
*B	5293268	MEDU	06/02/2016	Updated to new template.
*C	5848665	HARA	08/17/2017	Updated logo and copyright.

Worldwide Sales and Design Support

Cypress maintains a worldwide network of offices, solution centers, manufacturer's representatives, and distributors. To find the office closest to you, visit us at [Cypress Locations](#).

Products

ARM® Cortex® Microcontrollers	cypress.com/arm
Automotive	cypress.com/automotive
Clocks & Buffers	cypress.com/clocks
Interface	cypress.com/interface
Internet of Things	cypress.com/iot
Memory	cypress.com/memory
Microcontrollers	cypress.com/mcu
PSoC	cypress.com/psoc
Power Management ICs	cypress.com/pmic
Touch Sensing	cypress.com/touch
USB Controllers	cypress.com/usb
Wireless Connectivity	cypress.com/wireless

PSoC® Solutions

[PSoC 1](#) | [PSoC 3](#) | [PSoC 4](#) | [PSoC 5LP](#) | [PSoC 6](#)

Cypress Developer Community

[Forums](#) | [WICED IOT Forums](#) | [Projects](#) | [Videos](#) | [Blogs](#) | [Training](#) | [Components](#)

Technical Support

cypress.com/support

PSoC is a registered trademark and PSoC Creator is a trademark of Cypress Semiconductor Corporation.



Cypress Semiconductor
198 Champion Court
San Jose, CA 95134-1709

© Cypress Semiconductor Corporation, 2013-2017. This document is the property of Cypress Semiconductor Corporation and its subsidiaries, including Spansion LLC ("Cypress"). This document, including any software or firmware included or referenced in this document ("Software"), is owned by Cypress under the intellectual property laws and treaties of the United States and other countries worldwide. Cypress reserves all rights under such laws and treaties and does not, except as specifically stated in this paragraph, grant any license under its patents, copyrights, trademarks, or other intellectual property rights. If the Software is not accompanied by a license agreement and you do not otherwise have a written agreement with Cypress governing the use of the Software, then Cypress hereby grants you a personal, non-exclusive, nontransferable license (without the right to sublicense) (1) under its copyright rights in the Software (a) for Software provided in source code form, to modify and reproduce the Software solely for use with Cypress hardware products, only internally within your organization, and (b) to distribute the Software in binary code form externally to end users (either directly or indirectly through resellers and distributors), solely for use on Cypress hardware product units, and (2) under those claims of Cypress's patents that are infringed by the Software (as provided by Cypress, unmodified) to make, use, distribute, and import the Software solely for use with Cypress hardware products. Any other use, reproduction, modification, translation, or compilation of the Software is prohibited.

TO THE EXTENT PERMITTED BY APPLICABLE LAW, CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS DOCUMENT OR ANY SOFTWARE OR ACCOMPANYING HARDWARE, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. To the extent permitted by applicable law, Cypress reserves the right to make changes to this document without further notice. Cypress does not assume any liability arising out of the application or use of any product or circuit described in this document. Any information provided in this document, including any sample design information or programming code, is provided only for reference purposes. It is the responsibility of the user of this document to properly design, program, and test the functionality and safety of any application made of this information and any resulting product. Cypress products are not designed, intended, or authorized for use as critical components in systems designed or intended for the operation of weapons, weapons systems, nuclear installations, life-support devices or systems, other medical devices or systems (including resuscitation equipment and surgical implants), pollution control or hazardous substances management, or other uses where the failure of the device or system could cause personal injury, death, or property damage ("Unintended Uses"). A critical component is any component of a device or system whose failure to perform can be reasonably expected to cause the failure of the device or system, or to affect its safety or effectiveness. Cypress is not liable, in whole or in part, and you shall and hereby do release Cypress from any claim, damage, or other liability arising from or related to all Unintended Uses of Cypress products. You shall indemnify and hold Cypress harmless from and against all claims, costs, damages, and other liabilities, including claims for personal injury or death, arising from or related to any Unintended Uses of Cypress products.

Cypress, the Cypress logo, Spansion, the Spansion logo, and combinations thereof, WICED, PSoC, CapSense, EZ-USB, F-RAM, and Traveo are trademarks or registered trademarks of Cypress in the United States and other countries. For a more complete list of Cypress trademarks, visit cypress.com. Other names and brands may be claimed as property of their respective owners.