



Please note that Cypress is an Infineon Technologies Company.

The document following this cover page is marked as “Cypress” document as this is the company that originally developed the product. Please note that Infineon will continue to offer the product to new and existing customers as part of the Infineon product portfolio.

Continuity of document content

The fact that Infineon offers the following product as part of the Infineon product portfolio does not lead to any changes to this document. Future revisions will occur when appropriate, and any changes will be set out on the document history page.

Continuity of ordering part numbers

Infineon continues to support existing part numbers. Please continue to use the ordering part numbers listed in the datasheet for ordering.

How to Design a Power Management System with S6BP401A

Author: Yukinori Maekawa

Associated Part Family: S6BP401A


Related Documents: [S6BP401A Datasheet](#)

AN98649 explains how to select components and PCB layout guidelines for a power management system with S6BP401A, Cypress' 6-channel power management IC (PMIC).

1 Introduction

Cypress' S6BP401A is a PMIC for automotive advanced driver assistance systems (ADAS). It includes a 4-channel, step-down, 2.1-MHz DC/DC converter (DD1, DD2, DD3, and DD4), a 2-channel low-drop regulator (LDO; LDO1 and LDO2), and a watchdog timer as shown in [Figure 1](#). S6BP401A enables you to design an ADAS system with minimal number of parts. The supply voltages of the power system that uses S6BP401A are high-precision, and S6BP401A has a power-good function and a watchdog timer function. Therefore, S6BP401A, which is compliant with AEC-Q100, provides a high-reliability power system in automotive systems.

Figure 1. Block Diagram of the Power Management System

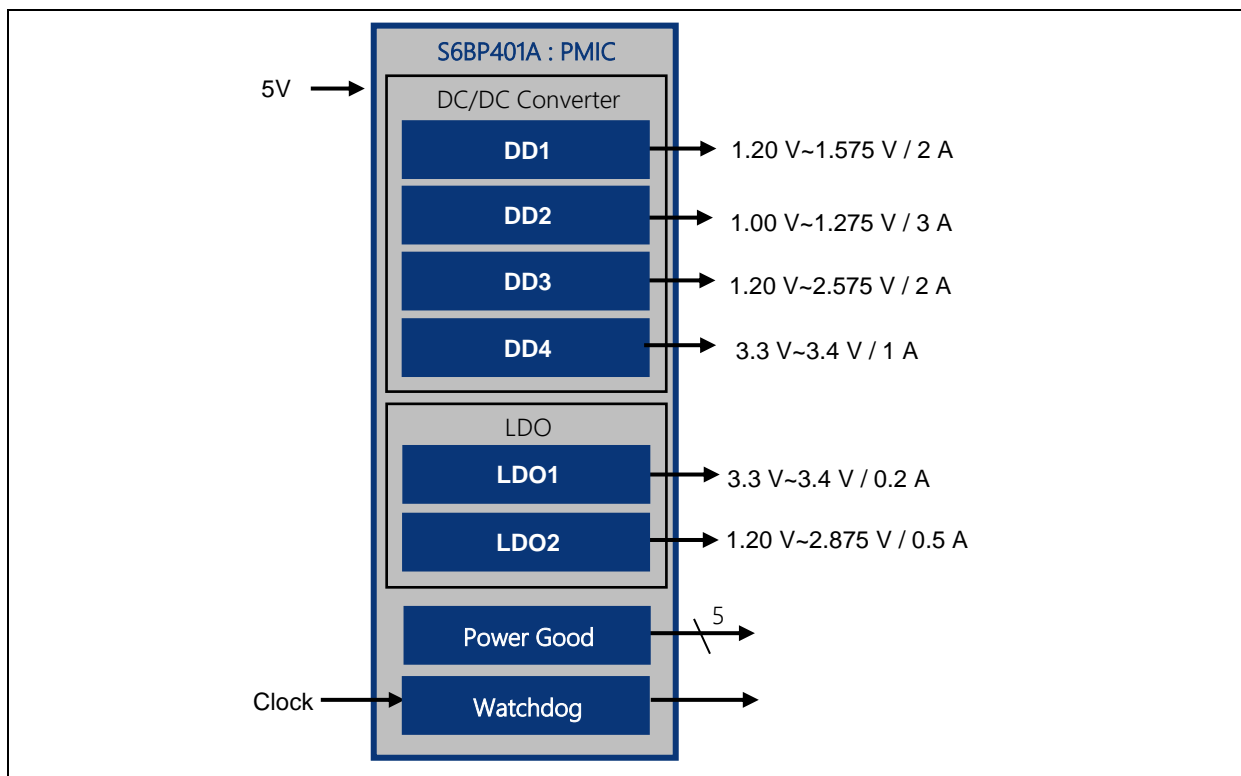


2 Components Selection

2.1 DC/DC Converter (DD1, DD2, DD3, and DD4) Parts Selection

DDx (where x=1, 2, 3, or 4) is a channel of DC/DC converter of PMIC. Select all components shown in Figure 2, which shows the DC/DC Converter section of an example circuit that uses S6BP401A.

Figure 2. Connection of the DC/DC Converter

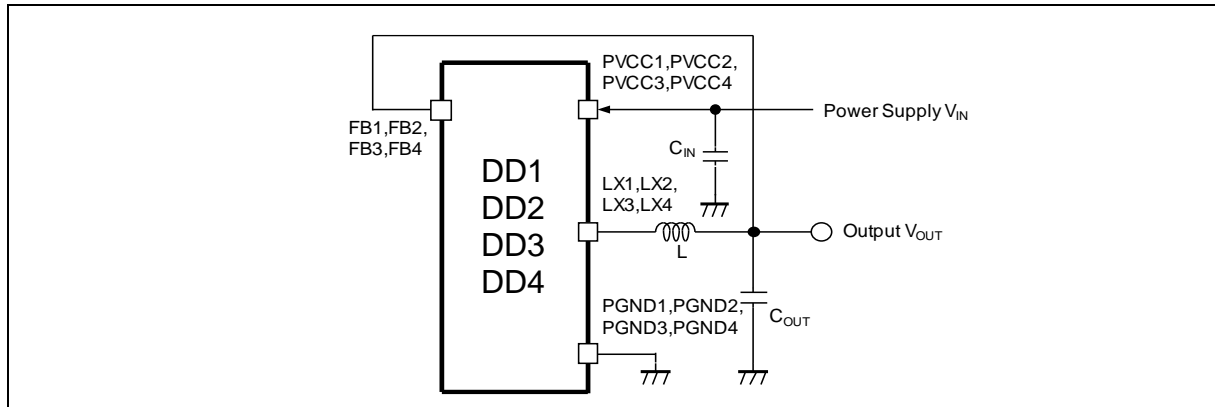

PVCCx, Lx, FBx, PGNDx (where x = 1, 2, 3, or 4) are terminal names of PMIC (see the [datasheet](#)).

2.1.1 Inductor (L)

Generally, the inductance of the coil is selected along with the value of the E6 series. Normally, you do not need to design an inductor for a power management system based on the S6BP401A device because it is designed to operate efficiently with a 1.5- μ H external inductor. At the same time, you should calculate the maximum current value to confirm whether the electric current that flows to the inductor is within the rated parameters for the inductor by using Equation 1.

Equation 1

$$I_{L_MAX} \geq I_{OUT_MAX} + \frac{\Delta I_L}{2}, \Delta I_L = \frac{V_{IN} - V_{OUT}}{L} \times \frac{V_{OUT}}{V_{IN} \times f_{OSC}}$$

Where:

I_{L_MAX} : Rated current of inductor (A)

I_{OUT_MAX} : Maximum load current (A)

ΔI_L : Ripple current peak-to-peak value of inductor (A)

L: Inductance of inductor (H)

V_{IN} : Power supply voltage (V)

V_{OUT} : Output setting voltage (V)

f_{OSC} : Switching frequency (Hz)

2.1.2 Input Capacitor (C_{IN})

A ceramic capacitor that has a low equivalent series resistance (ESR), typically less than 10 m Ω , and excellent frequency characteristics (the capacitance is not reduced up to the switching frequency), should be used. Generally, the capacitance is selected along with the value of the E6 series. The recommended value is 10 μ F. Ensure that $V_{CIN} > V_{IN}$, where V_{CIN} is the rated voltage of input capacitor (V) and V_{IN} is the power supply voltage (V).

2.1.3 Output Capacitor (C_{OUT})

A ceramic capacitor that has a low ESR and excellent frequency characteristics should be used. Table 1 lists the recommended capacitance values for each DC/DC converter channel of the device:

Table 1. Output Capacitance List

DD1	DD2	DD3	DD4
22 μ F (2 nos.)	22 μ F (3 nos.)	22 μ F (2 nos.)	22 μ F (2 nos.)


When you consider a ceramic capacitor, you should take into account the reduction of capacitance due to DC bias characteristics of the capacitor itself. Generally, a large-size capacitor has a stable DC bias characteristic. Ensure that

$V_{COUT} > V_{OUT}$, where V_{COUT} is the rated voltage of output capacitor (V); V_{OUT} is the output setting voltage (V).

2.2 LDO (LDO1 and LDO2) Parts Selection

LDO1 and LDO2 are channels of the LDO of the PMIC. Figure 3 shows the LDO section of an example circuit that uses the S6BP401A power management solution. You have to select each component in this figure.

Figure 3. Connection of the LDO

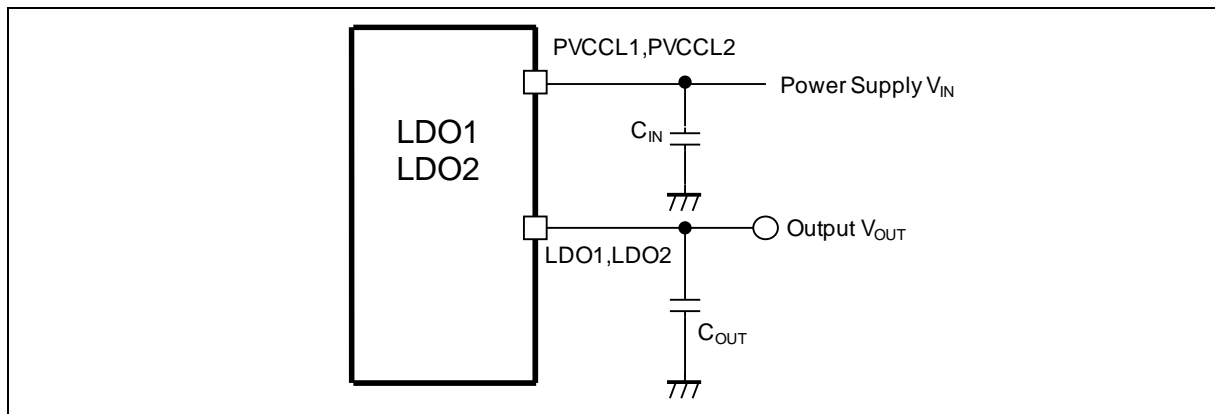

PVCCLx, LDOx (where x = 1 or 2) is terminal name of PMIC (see the [datasheet](#)).

2.2.1 Input Capacitor (C_{IN}), Output Capacitor (C_{OUT})

A ceramic capacitor that has low ESR and excellent frequency characteristics should be used. Table 2 lists the recommended capacitance values.

Table 2. Output Capacitance List

	LDO1	LDO2
Input capacitor	1 μ F	1 μ F
Output capacitor	1 μ F	10 μ F

Calculate the necessary rated voltage of the capacitor by the following formula.

$$V_{CIN} > V_{IN}, V_{COUT} > V_{OUT}$$

Where:

V_{CIN} : Rated voltage of input capacitor (V)

V_{IN} : Power supply voltage (V)

V_{COUT} : Rated voltage of output capacitor (V)

V_{OUT} : Output setting voltage (V)

2.3 Common Parts Selection

2.3.1 VCC and VREG Bypass Capacitor

VCC and VREG that is terminal of PMIC (see the [datasheet](#)) need a bypass capacitor. A ceramic capacitor that has a low ESR and excellent frequency characteristics should be used. The recommended value for these capacitors is 1 μF . Calculate the necessary rated voltage of the capacitor by using the following formula.

Equation 2

$$V_{CVCC} > V_{IN}, V_{CVREG} > V_{VREG}$$

Where:

V_{CVCC} : Rated voltage of VCC bypass capacitor (V)

V_{IN} : Power supply voltage (V)

V_{CVREG} : Rated voltage of VREG bypass capacitor (V)

V_{VREG} : VREG voltage (V)

2.3.2 PG1, PG2, PG3, PG4, PGL2 and RST Pull-Up Resistor

PGx (where x = 1, 2, 3, or 4), PGL2, and RST terminals of the PMIC need a pull-up resistor if the design uses the power good monitor or the watchdog function (see the [datasheet](#) for more information on each function). When you select the value for pull-up resistance, you should consider the leakage current (less than 1 μA) and the driving ability (3 mA) of each terminal. The resistance should be selected in the range of 2 k Ω to 100 k Ω .


3 PCB Layout Guidelines

This section explains how to design PCB layout for a power management system with S6BP401A.

3.1 DC/DC Converter (DD1, DD2, DD3, and DD4)

Figure 4 shows an example layout of the DC/DC converter (DD2) section shown in [Figure 2](#).

Figure 4. Layout Example of DD2

 

The switching components, consisting of an input capacitor (C_{IN}), IC, coil (L), and output capacitor (C_{OUT}), are placed close to each other. These components should be connected with a wide and short plane.

In particular, the current loop that includes the input capacitor (C_{IN}) and IC (PVCCx and PGNDx [where x = 1, 2, 3, or 4] terminal) should be carefully chosen to decrease the current loop. Another PCB layer, not a mounted components layer, should be used as a ground plane. The ground terminal of the switching component should be connected to this ground plane by through-holes that are put near the ground terminal of the switching component.


The feedback line from the FB_x (where x = 1, 2, 3, or 4) terminal of the IC should be connected individually to the terminal of the output capacitors. This wiring is sensitive to noise. It should be away from the pattern of the LX_x (where x = 1, 2, 3, or 4) terminal and the switching components.

There is leakage flux near a coil or the back of the PCB-mounted coil. Sensitive wiring and components should be located away from the coil or the back of the PCB-mounted coil.

3.2 LDO (LDO1 and LDO2)

Figure 5 shows an example layout of the LDO (LDO1) section shown in Figure 3.

Figure 5. Layout Example of LDO1

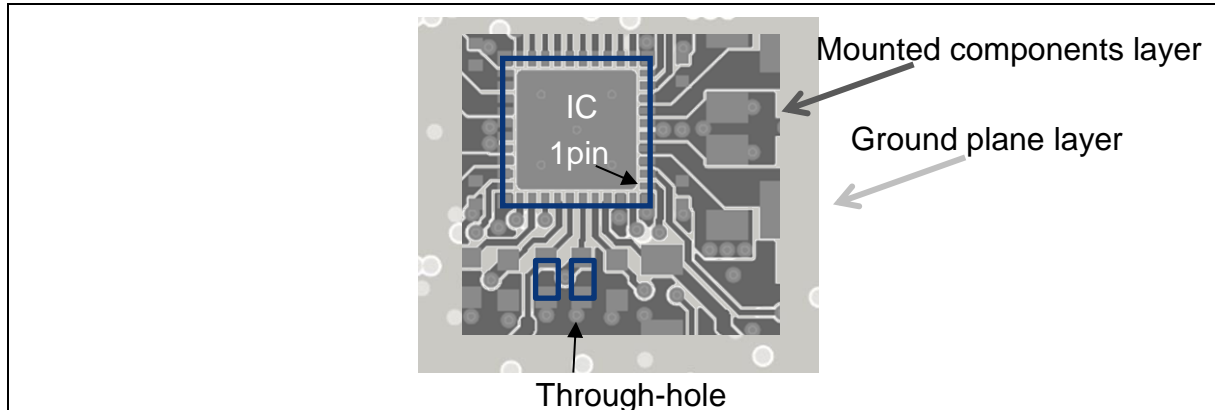


The input capacitor (C_{IN}) and output capacitor (C_{OUT}) should be placed close to the PVCC_{Lx} (where x = 1 or 2) terminal and the LDO_x (where x = 1 or 2) terminal of the IC. These components should be connected with a wide and short plane. The ground terminal of each capacitor should be connected to the ground plane of another layer by through-holes that are placed near the ground terminal of each capacitor.

3.3 Common (Ground, VCC, and VREG Bypass Capacitors)

Figure 6 shows an example layout of the common section.

Figure 6. Layout Example of Common Section

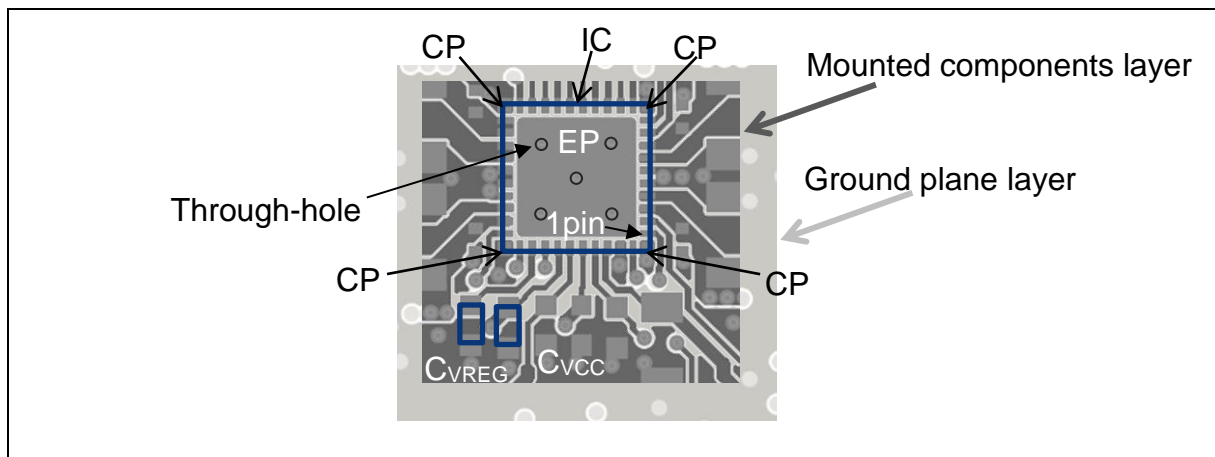

The exposed pad (EP) of PMIC should be connected to the ground plane that will be placed on the IC mounting surface. The EP should be connected to the ground plane of another layer for heat dissipation and stable operation purposes.

The VCC and VREG bypass capacitors (C_{VCC} , C_{VREG}) should be placed close to the VCC and VREG terminals of the IC. These components should be connected with a short line. The ground terminal of each capacitor and the corner pad (CP) of the IC should be connected to the ground plane of another layer by through-holes that are placed near each ground terminal of the capacitor and each CP terminal IC.

Document History

Document Title: AN98649 - How to Design a Power Management System with S6BP401A

Document Number: 001-98649

Revision	ECN	Orig. of Change	Submission Date	Description of Change
**	4880290	YMAE	08/11/2015	New application note
*A	5157275	YMAE	03/01/2016	Changed title. Added PCB layout guidelines.
*B	5815114	AESATMP8	07/13/2017	Updated logo and Copyright.
*C	6306566	YMAE	09/11/2018	Sunset review Updated template

Worldwide Sales and Design Support

Cypress maintains a worldwide network of offices, solution centers, manufacturer's representatives, and distributors. To find the office closest to you, visit us at [Cypress Locations](#).

Products

Arm® Cortex® Microcontrollers	cypress.com/arm
Automotive	cypress.com/automotive
Clocks & Buffers	cypress.com/clocks
Interface	cypress.com/interface
Internet of Things	cypress.com/iot
Memory	cypress.com/memory
Microcontrollers	cypress.com/mcu
PSoC	cypress.com/psoc
Power Management ICs	cypress.com/pmic

Touch Sensing	cypress.com/touch
USB Controllers	cypress.com/usb
Wireless Connectivity	cypress.com/wireless

PSoC® Solutions

[PSoC 1](#) | [PSoC 3](#) | [PSoC 4](#) | [PSoC 5LP](#) | [PSoC 6 MCU](#)

Cypress Developer Community

[Community](#) | [Projects](#) | [Videos](#) | [Blogs](#) | [Training](#)
| [Components](#)

Technical Support

cypress.com/support

All other trademarks or registered trademarks referenced herein are the property of their respective owners.



Cypress Semiconductor
198 Champion Court
San Jose, CA 95134-1709

© Cypress Semiconductor Corporation, 2015-2018. This document is the property of Cypress Semiconductor Corporation and its subsidiaries, including Spansion LLC ("Cypress"). This document, including any software or firmware included or referenced in this document ("Software"), is owned by Cypress under the intellectual property laws and treaties of the United States and other countries worldwide. Cypress reserves all rights under such laws and treaties and does not, except as specifically stated in this paragraph, grant any license under its patents, copyrights, trademarks, or other intellectual property rights. If the Software is not accompanied by a license agreement and you do not otherwise have a written agreement with Cypress governing the use of the Software, then Cypress hereby grants you a personal, non-exclusive, nontransferable license (without the right to sublicense) (1) under its copyright rights in the Software (a) for Software provided in source code form, to modify and reproduce the Software solely for use with Cypress hardware products, only internally within your organization, and (b) to distribute the Software in binary code form externally to end users (either directly or indirectly through resellers and distributors), solely for use on Cypress hardware product units, and (2) under those claims of Cypress's patents that are infringed by the Software (as provided by Cypress, unmodified) to make, use, distribute, and import the Software solely for use with Cypress hardware products. Any other use, reproduction, modification, translation, or compilation of the Software is prohibited.

TO THE EXTENT PERMITTED BY APPLICABLE LAW, CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS DOCUMENT OR ANY SOFTWARE OR ACCOMPANYING HARDWARE, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. No computing device can be absolutely secure. Therefore, despite security measures implemented in Cypress hardware or software products, Cypress does not assume any liability arising out of any security breach, such as unauthorized access to or use of a Cypress product. In addition, the products described in these materials may contain design defects or errors known as errata which may cause the product to deviate from published specifications. To the extent permitted by applicable law, Cypress reserves the right to make changes to this document without further notice. Cypress does not assume any liability arising out of the application or use of any product or circuit described in this document. Any information provided in this document, including any sample design information or programming code, is provided only for reference purposes. It is the responsibility of the user of this document to properly design, program, and test the functionality and safety of any application made of this information and any resulting product. Cypress products are not designed, intended, or authorized for use as critical components in systems designed or intended for the operation of weapons, weapons systems, nuclear installations, life-support devices or systems, other medical devices or systems (including resuscitation equipment and surgical implants), pollution control or hazardous substances management, or other uses where the failure of the device or system could cause personal injury, death, or property damage ("Unintended Uses"). A critical component is any component of a device or system whose failure to perform can be reasonably expected to cause the failure of the device or system, or to affect its safety or effectiveness. Cypress is not liable, in whole or in part, and you shall and hereby do release Cypress from any claim, damage, or other liability arising from or related to all Unintended Uses of Cypress products. You shall indemnify and hold Cypress harmless from and against all claims, costs, damages, and other liabilities, including claims for personal injury or death, arising from or related to any Unintended Uses of Cypress products.

Cypress, the Cypress logo, Spansion, the Spansion logo, and combinations thereof, WICED, PSoC, CapSense, EZ-USB, F-RAM, and Traveo are trademarks or registered trademarks of Cypress in the United States and other countries. For a more complete list of Cypress trademarks, visit cypress.com. Other names and brands may be claimed as property of their respective owners.