

Using Delta-Sigma Can Be As Easy As ADC (Part 4)

By Dave Van Ess, Applications Engineering Member of Technical Staff, Cypress Semiconductor Corp.


Based on the amount of e-mail I received after Part 3 of this series, many of you have already guessed that an incremental integrator is really just a delta-sigma modulator (DSM). Well, you're right! It actually is a continuous-time delta-sigma modulator. "Continuous time" comes from the fact that the integrator comprises resistors, a capacitor, and an op amp.

Most commercial DSMs are made with switched capacitor technology. I decided to explain continuous time because most engineers that are unfamiliar with DSM theory are more comfortable with linear circuits and Laplace transforms than they are with switched capacitors and z transforms. Switched capacitors will be a subject for a future column.

THE DETAILS

A DSM must have a difference (delta) circuit, an integrate or accumulate (sigma) circuit, and a quantization (modulation) circuit consisting of an ADC and a DAC. Figure 1 shows that the increment integrator is a DSM. The op-amp feedback causes the quantized output to be subtracted (?) from the input, and the result is integrated (S). The comparator on the output serves as a singlebit ADC and is the density output. This digital output controls the reference MUX, serving as a single DAC, resulting in a quantized (M) feedback signal.

 1. In this DSM, the op-amp feedback causes the quantized output to be subtracted from the input, and the result is integrated.




Suppose the references are ± 1 V. A 0.1-V integrator output results in a 1-V quantized output. This can be seen as 0.1 V with a 0.9 quantization error. A quantized -0.3 is -1 V or the addition of a -0.7 -V quantization error. Bearing this in mind, a DSM can be considered an integrator with a quantization noise source added to its output. Figure 1 shows this model of quantization noise.

Setting the RC time constant to match that of the sample clock ($RC = 1/f_s$) results in Equation 1, relating the output voltage to the input signal and quantization error:

$$V_{OUT} = -V_{IN} \times \frac{1}{1 + \frac{s}{f_s}} + e_Q \frac{\frac{s}{f_s}}{1 + \frac{s}{f_s}}$$

 The output is the sum of the low pass filtered input signal and the high pass filtered quantization noise. The relative amplitude of each is plotted as a function of frequency (*Fig. 2*). The plot clearly shows that the quantization noise has been pushed (shaped) toward the higher end of the spectrum. At a fairly low frequency, its relative response is roughly linear (*Equation 2*):



2. As a DSM's noise frequency relative to f_s increases, the quantization noise's relative amplitude increases, while the signal's relative amplitude decreases.

$$n(f) \approx \frac{e_{rms}}{\sqrt{\frac{f_s}{2}}} \times \frac{2\pi f}{f_s}; f \ll f_s$$

The lower the frequency, the less quantization noise there is. The plot has a marker set to some frequency far less than the sample rate (f_0). The amount of noise below that value is small, and the signal to noise ratio (SNR) is large. Making the bandwidth smaller increases the SNR ratio. To calculate the total quantization noise, each bit of the noise left in this band must be added (*Equation 3*):



$$\eta_0 = \sqrt{\int_0^{f_0} \eta(f)^2 df} \approx \sqrt{\frac{8}{3} \pi \times e_{rms} \times \left(\frac{f_s}{f_0}\right)^2} = \sqrt{\frac{8}{3} \pi \times e_{rms} \times OSR^{-2}}; f \ll f_s$$

The noise is accumulated using root square sum. Note that the total noise is inversely proportional to $f_0^{3/2}$. Lower the bandwidth by two octaves (12 dB), and the noise goes down by a factor of eight (18 dB). With the proper digital filter, it is possible to achieve 9-dB/octave performance from such a delta-sigma modulator.

The proper filter is called a decimator. The word “decimate” is Roman in origin, meaning to reduce by a tenth. Decimation was an extreme punishment given to the Roman Legions when they had upset their leaders. The men would be divided into groups of 10, decide which member of their group would be executed, and carry out the execution. The survivors would then be put on a diet of barley and water for a month. These remaining 90% came away highly motivated to meet the future expectations of their leaders. (In these more enlightened times, we still carry on this tradition. We call it “layoffs.”)

This decimator is a digital finite impulse response (FIR) filter that takes the input at f_s and provides a filtered output at f_0 . The ratio of these two frequencies is called the oversample ratio (OSR) or decimation value. The bandwidth limit in Figure 2 is for an OSR of 64. The specifics of the filter are not important for this discussion. Digital decimator filter design is a subject better suited for a future column.

Now, 9-dB/octave certainly is better than the 6 dB/octave produced by the incremental ADC. An incremental ADC with a 1-Msample/s clock and 16-bit resolution has an output rate of 15 samples/s. Take the same DS modulator, and with the proper decimator, you get 16 bits of resolution at 488 samples/s. This is an improvement—not great, but definitely an improvement.

My next column will explain multiple-stage delta-sigma modulators and show how to get resolution enhancements of 15, 21, and 27 dB per octave and more.

Cypress Semiconductor
198 Champion Court
San Jose, CA 95134-1709
Phone: 408-943-2600
Fax: 408-943-4730
<http://www.cypress.com>

© Cypress Semiconductor Corporation, 2007. The information contained herein is subject to change without notice. Cypress Semiconductor Corporation assumes no responsibility for the use of any circuitry other than circuitry embodied in a Cypress product. Nor does it convey or imply any license under patent or other rights. Cypress products are not warranted nor intended to be used for medical, life support, life saving, critical control or safety applications, unless pursuant to an express written agreement with Cypress. Furthermore, Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress products in life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

PSoC Designer™, Programmable System-on-Chip™, and PSoC Express™ are trademarks and PSoC® is a registered trademark of Cypress Semiconductor Corp. All other trademarks or registered trademarks referenced herein are property of the respective corporations.

This Source Code (software and/or firmware) is owned by Cypress Semiconductor Corporation (Cypress) and is protected by and subject to worldwide patent protection (United States and foreign), United States copyright laws and international treaty provisions. Cypress hereby grants to licensee a personal, non-exclusive, non-transferable license to copy, use, modify, create derivative works of, and compile the Cypress Source Code and derivative works for the sole purpose of creating custom software and/or firmware in support of licensee product to be used only in conjunction with a Cypress integrated circuit as specified in the applicable agreement. Any reproduction, modification, translation, compilation, or representation of this Source Code except as specified above is prohibited without the express written permission of Cypress.

Disclaimer: CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS MATERIAL, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. Cypress reserves the right to make changes without further notice to the materials described herein. Cypress does not assume any liability arising out of the application or use of any product or circuit described herein. Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress' product in a life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

Use may be limited by and subject to the applicable Cypress software license agreement.