

Five Building Blocks of an Efficient High Brightness LED Driver


By Rakesh Reddy, application engineer, Cypress Semiconductor Corp.

As High Brightness LEDs (HBLEDs) penetrate all avenues of the lighting market, constant current drivers are being offered by various semiconductor manufacturers. Only by choosing a driver IC capable of meeting the flexibility and control required by today's applications can the true potential of these devices be unleashed. In theatrical lighting for example, it is necessary to facilitate a high dimming resolution while dynamically adjusting the current to account for fluctuating power sources and operating temperature. Since the quality of light output is intrinsically tied to the capability of the LED driver, it is important to choose a system that has the right specifications.

Today's HBLEDs typically have a nominal current rating of 300mA to 700mA. As the envelope of light output is pushed, devices requiring more than an Ampere are appearing in the market. In all LEDs, due to the voltage-current relationship and the binning approach used by manufacturers, a constant current source is used for accurate control of the light output. Choosing the right constant current regulator depends on the operating voltage of load and source, desired efficiency, and the cost and size of the system. A high power resistor in series with LEDs would be the simplest. Since a resistor alone cannot adapt to changing source voltages or the non-linear VI characteristics of an LED, a closed loop system that changes the resistance based on output current may be used. In either case, the energy not used by the LED is dissipated as heat by the linear regulator leading to an inefficient system. In most HBLED applications, switching regulators offer better efficiency over a wide range of operating voltages.


HBLED lighting fixtures seeking to replace incandescent and fluorescent bulbs must provide better efficiency and quality of light while maintaining low costs. An integrated switching regulator used in lighting applications must require minimal external components and have good current regulation. While switching regulators can have diverse forms, they all operate using the same principle of moving small quantities of energy from the source to the load. The efficiency of the conversion has little dependence on the input voltage. However, the topology chosen depends on the voltage conversion required. A Buck topology allows the source voltage to be greater than the load voltage and is typically used for driving LEDs.

The main control system in any buck regulator is the hysteretic controller. This block regulates the current through the inductor by turning on a switch when it is below the lower threshold and vice versa. A shunt resistor is a convenient method of sensing the current and by pairing it with a differential Current Sense Amplifier (CSA), a smaller resistance can be used minimizing power losses. The feedback from the CSA is used by the analog circuitry of the controller. These blocks can be arranged in various combinations and in figure 1, different LED colors differentiate the topologies.

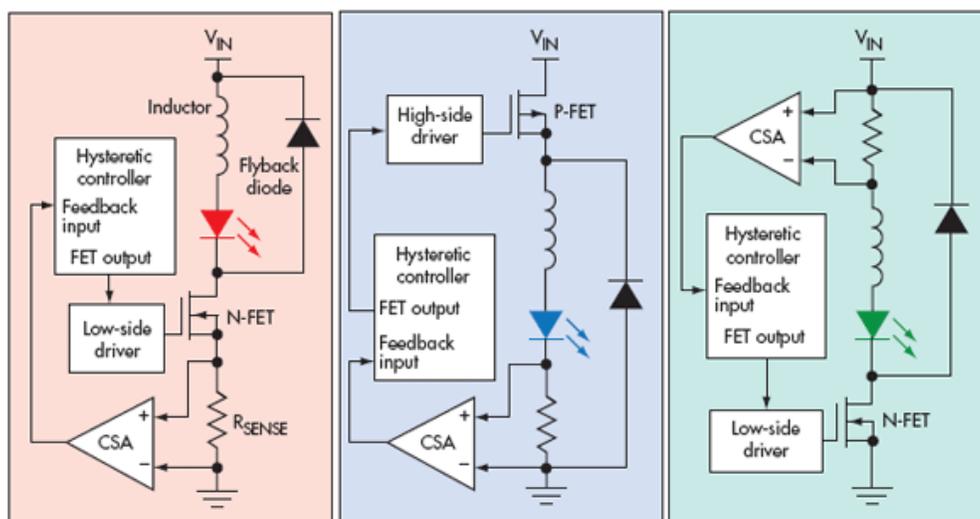

I. Three unique topologies may allow the implementation of a buck regulator.

Figure 3 shows a technique for such a CSA that cascades a differential amplifier, level shifter and a secondary amplifier stage. It operates by creating a current I_{sense} in the low voltage realm that is proportional to V_{sense} on the high side. An additional amplifier with adjustable gain can be used to obtain a signal whose voltage matches that obtained from the reference DACs in the Hysteretic Controller. A high gain setting in the CSA allows the use of low value sense resistors minimizing the power losses. A choice between 20 and 100 will address the requirements of most HLED designs. Since the CSA is sensing the rising and falling currents, it is important that sensor's bandwidth is greater than the switching frequency. When high bandwidth is not required, choosing a lower one will reduce the noise picked from the supply through the positive pin of the differential amplifier.

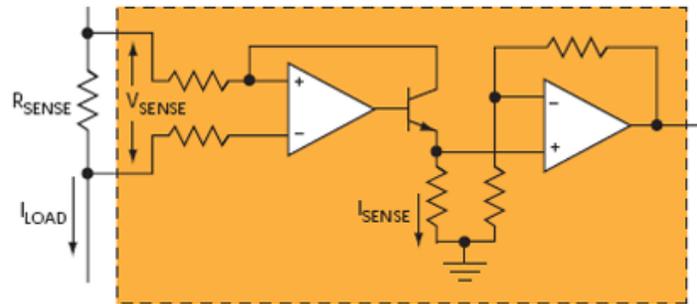

3. A two-stage CSA amplifies the differential high-side voltage while providing ground-referenced feedback to the hysteretic controller.

3) Gate Driver and FET

As the choice of gate driver and FET are intrinsically tied to the maximum switching frequency possible and efficiency of the system, they have to be chosen carefully after a trade off between cost, size and performance of the design. A FET with lesser R_{ds} will reduce conduction losses, and lesser gate capacitance will reduce switching losses. The gate driver must be able to drive the gate capacitance at the switching frequency desired. If the gate driver is not powerful enough, the ramps rate could be too slow causing the FET to operate in the inefficient linear region, and if it is too powerful, the FET could ring producing EMI emissions.

4) Modulator

The modulator's output provides the dimming signal to the hysteretic controller. A high output from the modulator produces constant current at the LED while a low relates to zero current. The choice of modulation scheme should allow for a high degree of resolution to harness the potential of LEDs. As the human eye can perceive small gradients at lower intensity levels, an 8-bit modulation scheme will create undesirable and perceptible steps in an extended fade sequence. A higher resolution of 12 to 16-bit modulator requires a clocking frequency allows for a smoother gradient. However, the modulator frequency must be high enough to allow for a refresh rate that is higher than the persistence of human vision. For example when using a 16-bit modulation at 700 Hz the modulator must be clocked at $700\text{Hz} * 65536 \text{ cnts} \approx 45\text{MHz}$. Today, different modulation schemes are available for driving LEDs. Pulse Width Modulation (PWM) involves representing the desired dimming quantity as a ratio of width of the pulse to the period of the pulse. Other modulation techniques like PriSM™ (Precise Illumination Signal Modulation) spread the dimming quantity in a pseudo-random fashion throughout the period of the pulse. Such a stochastic signal density modulation scheme spreads the energy throughout the spectrum reducing quasi peak emissions.

5) Trip Circuitry

Various scenarios require the driver element to halt the constant current hysteretic control loop. Operating under sudden input voltage fluctuations and temperature gradients can affect the longevity and performance of the LED engine. A trip circuitry comprising of a programmable DAC and comparator can produce the required logic pulse at the trip input of the hysteretic controller's logical AND function to hold the switch down.

Advancements in semiconductor technology are allowing for integration of these components into fast shrinking and inexpensive programmable controllers. The PowerPSoC™ family of parts contains hysteretic controller channels that can be setup to create various topologies to drive HLEDs. By coupling integrated drivers with an onboard microprocessor, the cost and form factor of a solution can be reduced with supplementary benefits associated with reduction in EMI emissions.



Cypress Semiconductor
198 Champion Court
San Jose, CA 95134-1709
Phone: 408-943-2600
Fax: 408-943-4730
<http://www.cypress.com>

© Cypress Semiconductor Corporation, 2007. The information contained herein is subject to change without notice. Cypress Semiconductor Corporation assumes no responsibility for the use of any circuitry other than circuitry embodied in a Cypress product. Nor does it convey or imply any license under patent or other rights. Cypress products are not warranted nor intended to be used for medical, life support, life saving, critical control or safety applications, unless pursuant to an express written agreement with Cypress. Furthermore, Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress products in life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

PSoC Designer™, Programmable System-on-Chip™, and PSoC Express™ are trademarks and PSoC® is a registered trademark of Cypress Semiconductor Corp. All other trademarks or registered trademarks referenced herein are property of the respective corporations.

This Source Code (software and/or firmware) is owned by Cypress Semiconductor Corporation (Cypress) and is protected by and subject to worldwide patent protection (United States and foreign), United States copyright laws and international treaty provisions. Cypress hereby grants to licensee a personal, non-exclusive, non-transferable license to copy, use, modify, create derivative works of, and compile the Cypress Source Code and derivative works for the sole purpose of creating custom software and or firmware in support of licensee product to be used only in conjunction with a Cypress integrated circuit as specified in the applicable agreement. Any reproduction, modification, translation, compilation, or representation of this Source Code except as specified above is prohibited without the express written permission of Cypress.

Disclaimer: CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS MATERIAL, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. Cypress reserves the right to make changes without further notice to the materials described herein. Cypress does not assume any liability arising out of the application or use of any product or circuit described herein. Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress' product in a life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

Use may be limited by and subject to the applicable Cypress software license agreement.